



**AMERICAN INTERNATIONAL UNIVERSITY–BANGLADESH (AIUB)**

**FACULTY OF SCIENCE & TECHNOLOGY**

**DEPARTMENT OF PHYSICS**

**PHYSICS 1 LAB**

**Spring 2021-2022**

**Section: B19, Group: 03**

**LAB REPORT ON**

**(a) Study of Ohm's law using unknown resistances.**

**(b) Determination of the equivalent resistances for series and parallel combinations of resistors.**

**Supervised By**

**Md. Saiful Islam**

**Submitted By**

Name	ID	Contribution
1. Sha Sultan Sowhan	22-47014-1	
2. Mahmuda Khatun	22-47016-1	
3. Farjana Yesmin Opi	22-47018-1	Dhongi meye kaj korena ekdom
4. Md. Abu Towsif	22-47019-1	

Date of Submission: **March 31, 2022**

## **TABLE OF CONTENTS**

<b>TOPICS</b>	<b><i>Page no.</i></b>
<b>I. Title Page</b>	<b>1</b>
<b>II. Table of Content</b>	<b>2</b>
<b>1. Theory</b>	<b>3</b>
<b>2. Apparatus</b>	<b>4</b>
<b>3. Procedure</b>	<b>4</b>
<b>4. Experimental Data</b>	<b>5,6</b>
<b>5. Analysis and Calculation</b>	<b>7,8</b>
<b>6. Result</b>	<b>9</b>
<b>7. Discussion</b>	<b>9</b>
<b>8. References</b>	<b>9</b>

## 1. Theory

Ohm's law states that the current through a conductor between two points is directly proportional to the voltage across those two points. Introducing the constant of proportionality, the resistance, one arrives at the usual mathematical equation that describes this relationship:

$$V = IR$$

where  $I$  is the current and  $V$  is the potential difference across the resistance  $R$

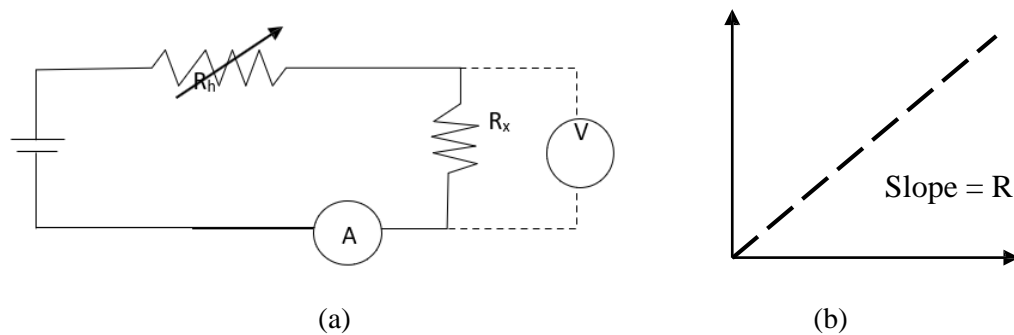


Figure 5.1: (a) Simple circuit to determine unknown resistance,  $R_x$  by using Ohm's law, ammeter (A) and voltmeter (V) are used to measure the current and potential drop in the circuit, variable resistor,  $R_h$  is used to change the current flow in the circuit (b) Slope of the  $V$  vs  $I$  graph gives the value of  $R$ .

When  $N$  number of resistors are connected in series and parallel connections their equivalent resistances  $R_s$  and  $R_p$  are calculated by the following two equations:

$$R_s = R_1 + R_2 + \dots + R_N$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$

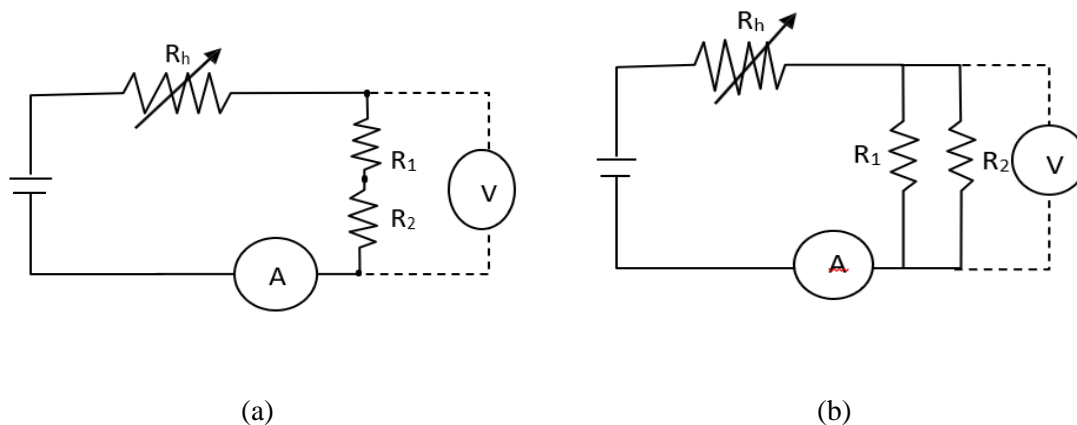


Figure 5.2: Series and parallel connections are shown for two resistors  $R_1$  and  $R_2$  in (a) and (b), respectively

## 2. Apparatus

1. Power Supply
2. Variable resistor
3. Ammeter
4. Voltmeter
5. Unknown resistors
6. Connecting wires

## 3. Procedure

1. First of all, we constructed above with 2 unknown resistances ( $R_1$  &  $R_2$ ).
2. By choosing  $R_h$  current not more than 1 A, we varied  $R_h$  to select 06 different currents through the circuit as measured by the ammeter  $A$ .
3. Then we measured the corresponding potential differences ( $V$ ) in the voltmeter.

## 4. Experimental Data



Table 1: Voltage current records for R<sub>1</sub> and R<sub>2</sub>



Resistors	Current I (A)	Voltage V (V)
R <sub>1</sub>	0.05	0.1546
	0.10	0.3109
	0.15	0.470
	0.20	0.608
	0.25	0.772
	0.30	0.922
R <sub>2</sub>	0.05	0.0478
	0.10	0.0967
	0.15	0.1429
	0.20	0.1923
	0.25	0.237
	0.30	0.2916

Table 2: Voltage current records for series and parallel connestions

Combination of $R_1$ & $R_2$	Current I (A)	Voltage V (v)
Series Combination	0.05	0.2116
	0.10	0.404
	0.15	0.613
	0.20	0.817
	0.25	0.999
	0.30	1.239
Parallel Combination	0.05	0.0365
	0.10	0.0733
	0.15	0.11
	0.20	0.1467
	0.25	0.1813
	0.30	0.2148

## 5. Analysis and Calculation

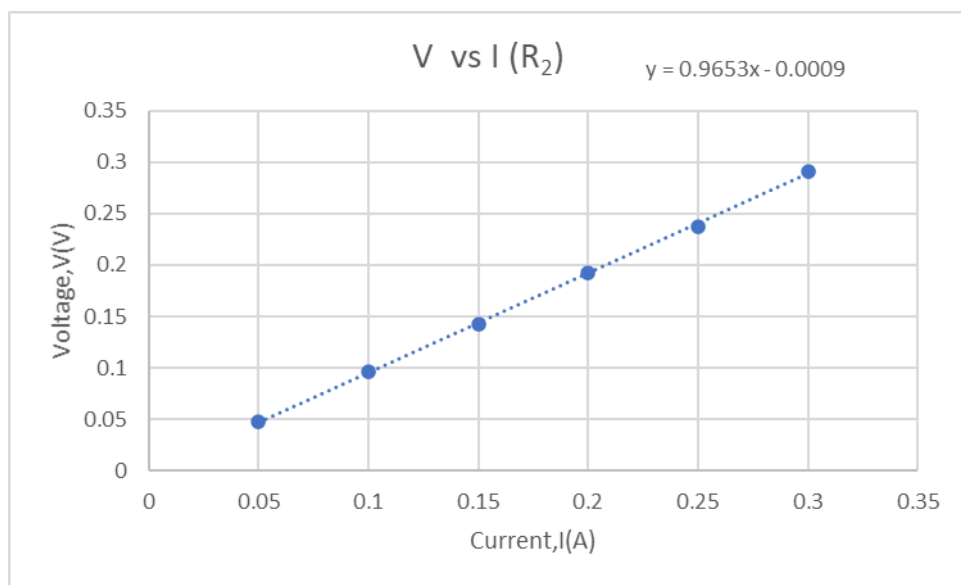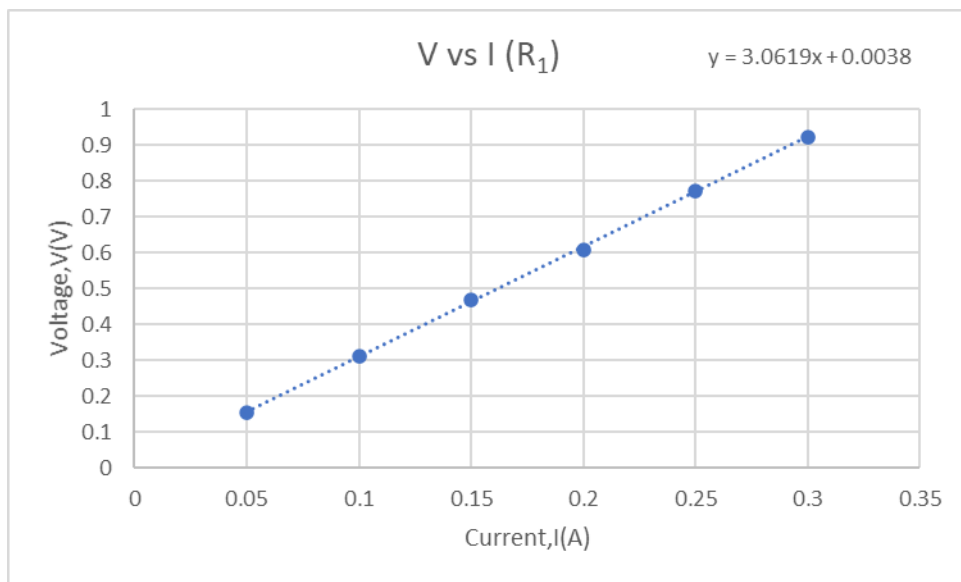

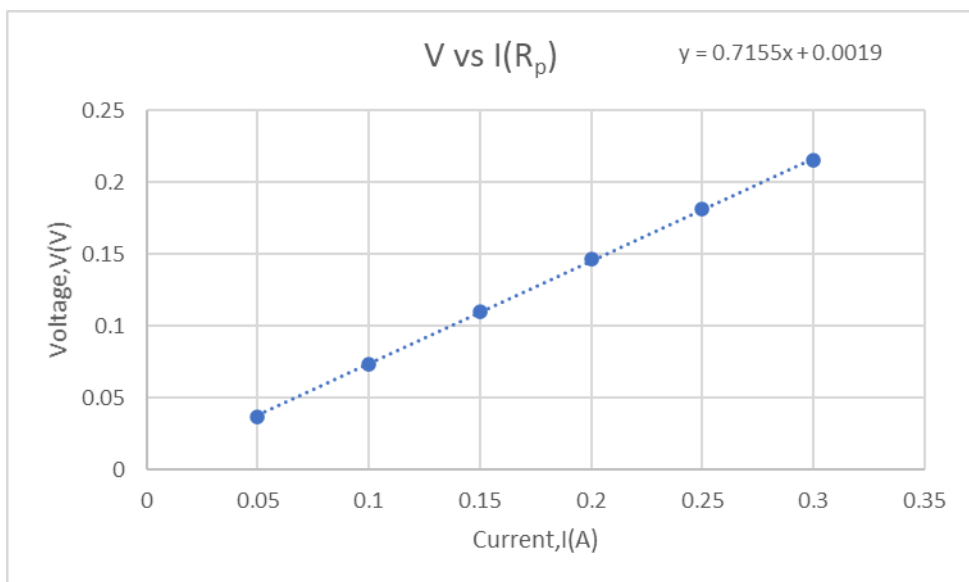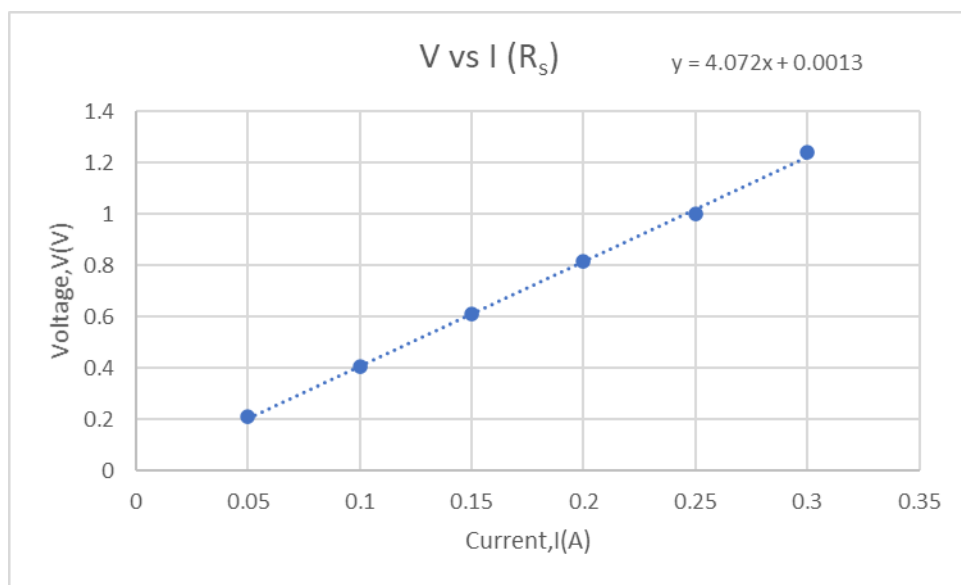



**Calculating the values of  $R_s$  and  $R_p$ :**

$$R_s = R_1 + R_2 = (3.0619 + 0.9653) \Omega$$

$$R_s = 4.0272 \Omega$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} = \left( \frac{1}{3.0619} + \frac{1}{0.9653} \right) = 1.3625 \Omega$$

$$R_p = \frac{1}{1.3625} = 0.7339 \Omega$$

## 6. Result

Resistances from the graphs		Calculated Values for $R_s$ and $R_p$ in ohms	Comments
Resistors	Values in Ohms		We got $R_s = 4.072 \Omega$ and $R_p = 0.7155 \Omega$ from the experiment. Hand calculated values, $R_s = 4.072 \Omega$ and $R_p = 0.7399 \Omega$ . So we can say that the experiment is verified
$R_1$	3.0619		
$R_2$	0.9653		
$R_s$	4.072	4.0272	
$R_p$	0.7155	0.7339	

## 7. Discussion

1. We got our values of  $R_s$  and  $R_p$  very close. But if you have taken more readings then our values would have been more accurate.
2. We were careful about making the graphs.
3. If there is a constant resistance in the circuit, the current is directly proportional to the voltage and will increase as the voltage increases.
4. We took every reading carefully as well as every calculation.

## 8. References

**Fundamental of Physics (10th Edition):** Ohm's Law (Chapter 26, page 756-759)