

LESSON 7

BOOK CHAPTER 25

CAPACITANCE

Capacitors in parallel combination:


V is same across all capacitors

Charge on each capacitor:

$$q_1 = C_1 V$$

$$q_2 = C_2 V$$

$$q_3 = C_3 V$$

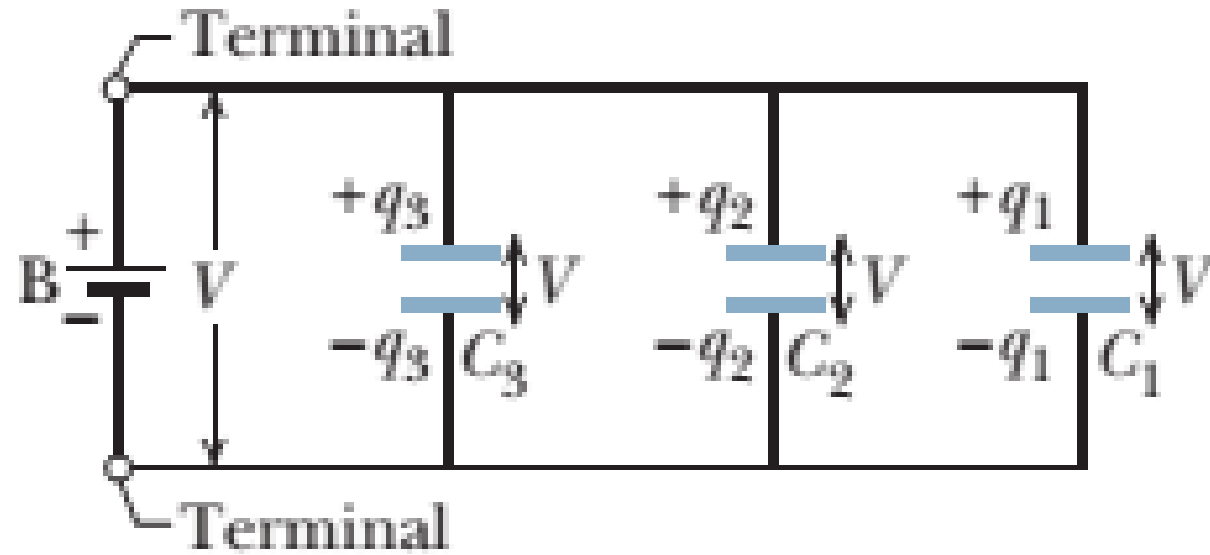


The total charge on the parallel combination is then

$$q = q_1 + q_2 + q_3 = (C_1 + C_2 + C_3)V$$

The equivalent capacitance, with the same total charge q and applied potential difference V as the combination, is then

$$C_{eq} = \frac{q}{V} = \frac{(C_1 + C_2 + C_3)V}{V} = C_1 + C_2 + C_3$$

$$C_{eq} = C_1 + C_2 + C_3$$

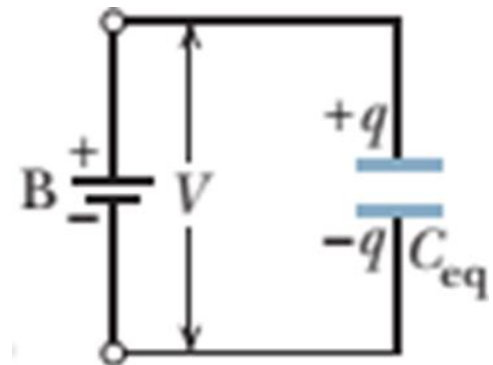

Capacitors in series combination:

q is same for all capacitors and voltages are different across capacitors.

Potential difference of each actual capacitor:

$$V_1 = \frac{q}{C_1} \quad V_2 = \frac{q}{C_2} \quad \text{And} \quad V_3 = \frac{q}{C_3}$$



The total potential difference V due to the battery is the sum of these three potential differences. Thus,

$$V = V_1 + V_2 + V_3 = q \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)$$

The equivalent capacitance is then

$$C_{eq} = \frac{q}{V} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$$
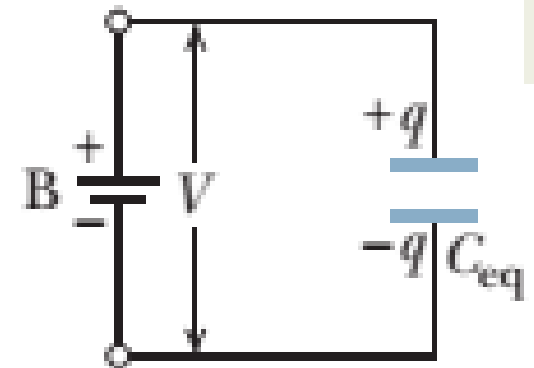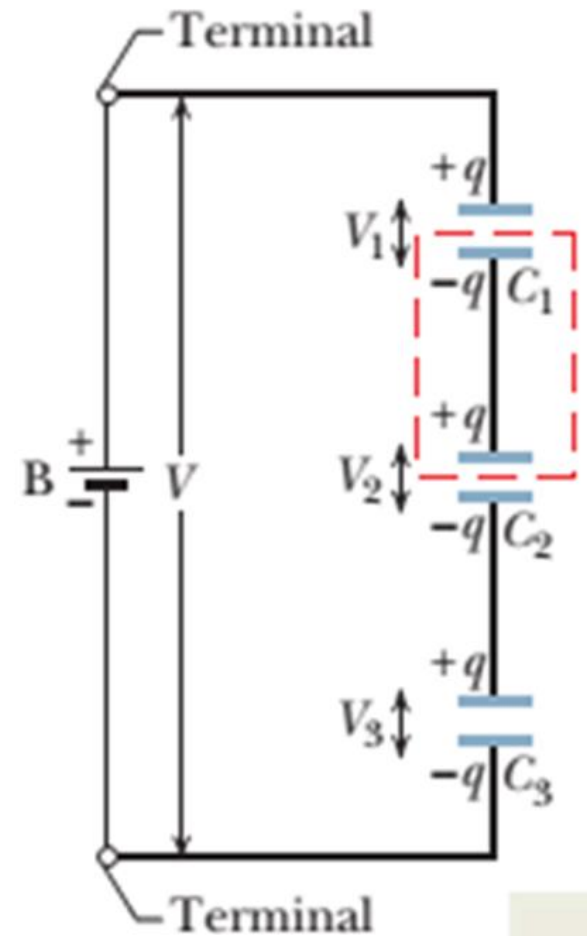
$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$



Problem 10 (Book chapter 25):

In the adjacent Figure, find the equivalent capacitance of the combination. Assume that C_1 is $10.00 \mu F$, C_2 is $5.00 \mu F$, and C_3 is $4.00 \mu F$.


Answer: **Step1:** C_1 and C_2 are in series

$$\frac{1}{C_{12}} = \frac{1}{C_1} + \frac{1}{C_2} \quad \text{or} \quad C_{12} = \frac{C_1 C_2}{C_2 + C_1}$$

$$C_{12} = \frac{(10)(5)}{5 + 10} = \frac{50}{15} = 3.33 \mu F$$

Step2: C_{12} and C_3 are in parallel

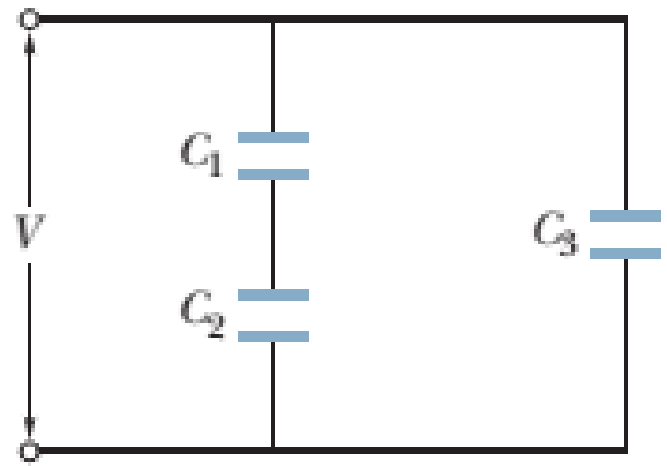
$$C_{123} = C_{12} + C_3 = 3.33 + 4 = 7.33 \mu F$$



Given

$$C_1 = 10 \mu F \quad C_2 = 5 \mu F$$

$$C_3 = 4 \mu F$$

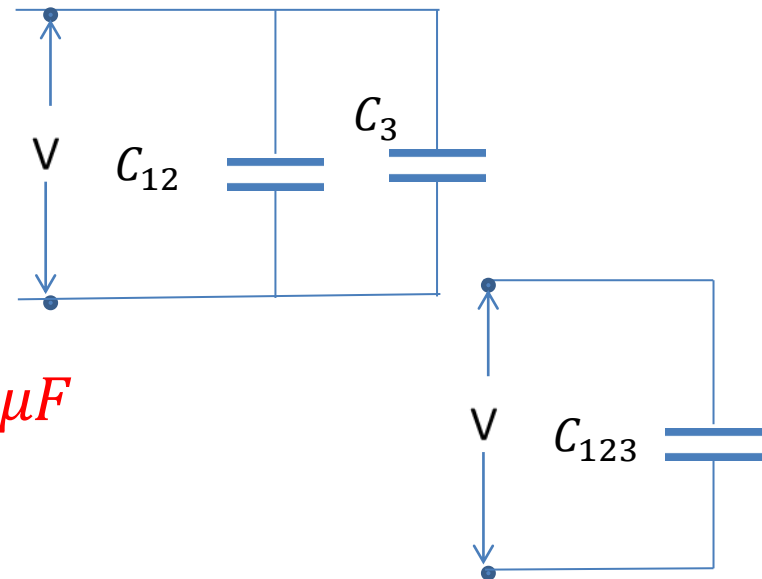

Problem 11 (Book chapter 25):

In the adjacent Figure, find the equivalent capacitance of the combination. Assume that C_1 is $10.00 \mu F$, C_2 is $5.00 \mu F$, and C_3 is $4.00 \mu F$.

Answer:

Step1: C_1 and C_2 are in parallel


$$C_{12} = C_1 + C_2 = 10 + 5 = 15 \mu F$$

Step2: C_{12} and C_3 are in series

$$\frac{1}{C_{123}} = \frac{1}{C_{12}} + \frac{1}{C_3} = \frac{C_3 + C_{12}}{(C_{12})(C_3)}$$

$$C_{123} = \frac{(C_{12})(C_3)}{C_3 + C_{12}}$$
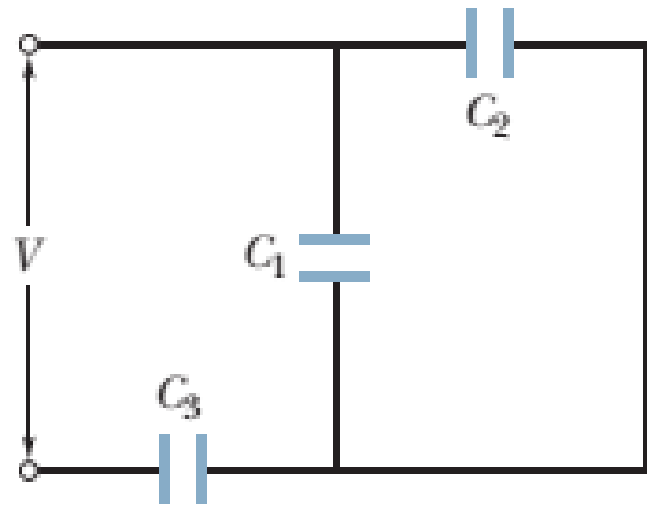
$$C_{123} = \frac{(15)(4)}{4 + 15} = \frac{60}{19} = 3.158 \mu F$$





Given

$$C_1 = 10 \mu F$$

$$C_2 = 5 \mu F$$

$$C_3 = 4 \mu F$$




$$C_{123} = ?$$

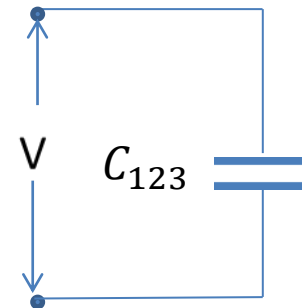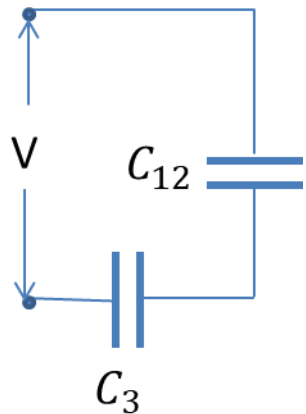

Sample Problem 25.02(a) (page 726): Find the equivalent capacitance for the combination of capacitances shown in Figure, across which potential difference V is applied.

Assume $C_1 = 12.0 \mu F$, $C_2 = 5.30 \mu F$, and $C_3 = 4.5 \mu F$.

Home Task

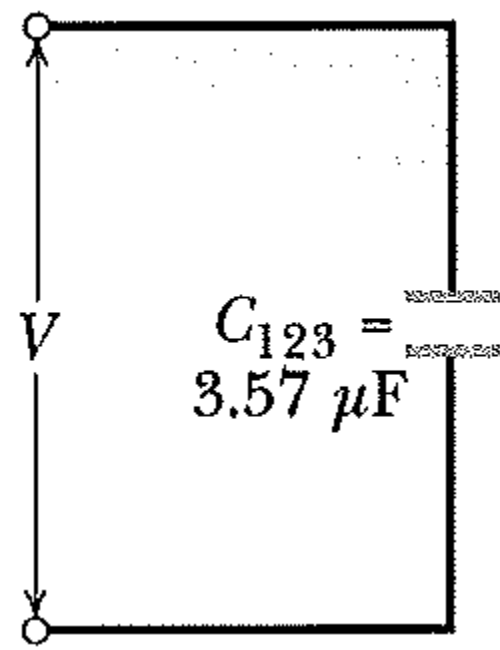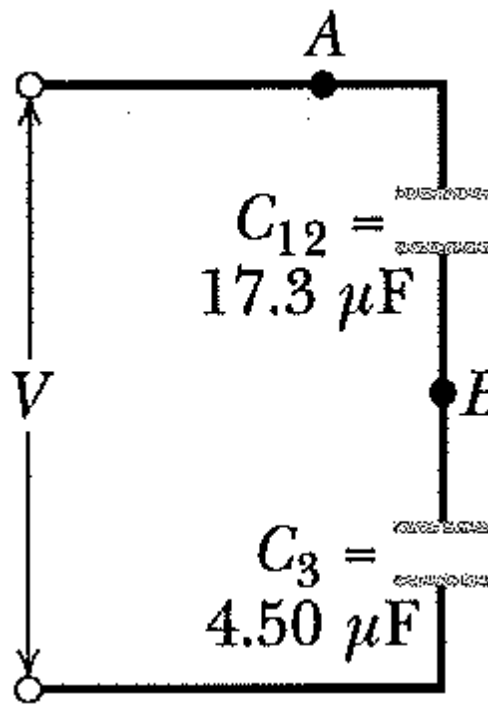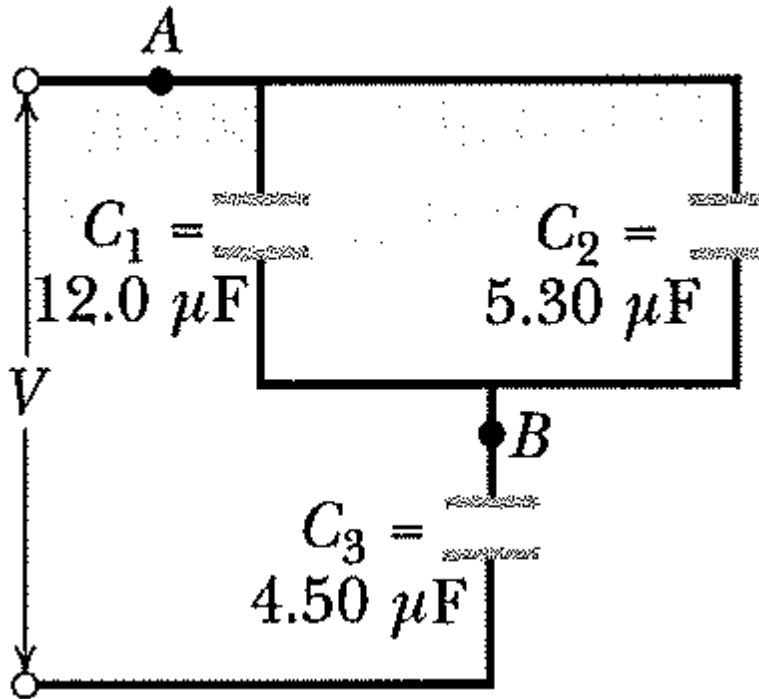


Step1: C_1 and C_2 are in parallel

$$C_{12} = C_1 + C_2 = 12 + 5.3 = 17.3 \mu F$$

Step2: C_{12} and C_3 are in series
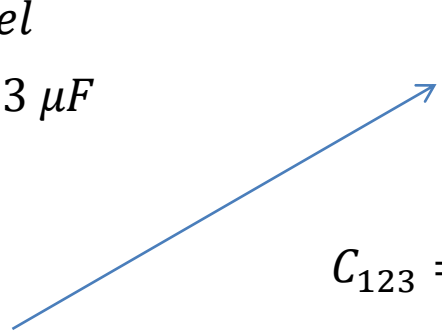
$$\frac{1}{C_{123}} = \frac{1}{C_{12}} + \frac{1}{C_3} = \frac{C_3 + C_{12}}{(C_{12})(C_3)}$$



$$C_{123} = \frac{(C_{12})(C_3)}{C_3 + C_{12}}$$

$$C_{123} = \frac{(17.3)(4.5)}{4.5 + 17.3} = \frac{77.85}{21.8} = 3.57 \mu F$$

Energy Stored in an Electric Field:

Suppose that, at a given instant, a charge q' has been transferred from one plate of a capacitor to the other. The potential difference V' between the plates at that instant will be $\frac{q'}{C}$. If an extra increment of charge dq' is then transferred, the increment of work required will be,

$$dW = V' dq' = \frac{q'}{C} dq'$$

The work required to bring the total capacitor charge up to a final value q is

$$W = \int_{q'=0}^{q'=q} dW = \frac{1}{C} \int_0^q q' dq' = \frac{q^2}{2C}$$

This work is stored as potential energy U in the capacitor, so

$$U = W = \frac{q^2}{2C} = \frac{(CV)^2}{2C} = \frac{1}{2} CV^2$$

Finally,

$$U = \frac{q^2}{2C}$$

OR

$$U = \frac{1}{2} CV^2$$

Energy Density:

In a parallel-plate capacitor, the electric field has the same value at all points between the plates. Thus, **the energy density u that is, the potential energy per unit volume** between the plates should also be uniform. We can find u by dividing the total potential energy by the volume Ad of the space between the plates. Thus

$$u = \frac{U}{Ad} = \left(\frac{1}{2}CV^2\right) \frac{1}{Ad}$$

For parallel plate capacitor, the capacitance can be expressed as

$$C = \frac{\epsilon_0 A}{d}$$

Therefore,

$$u = \left(\frac{1}{2}CV^2\right) \frac{1}{Ad} = \left(\frac{V^2}{2Ad}\right) \left(\frac{\epsilon_0 A}{d}\right) = \frac{\epsilon_0 V^2}{2d^2}$$

Finally,

$$u = \frac{1}{2} \epsilon_0 \left(\frac{V}{d}\right)^2$$

OR


$$u = \frac{1}{2} \epsilon_0 E^2$$

[since $V = Ed$]

Energy stored in an electric field:

$$q' = CV'$$

$$V' = \frac{q'}{C}$$

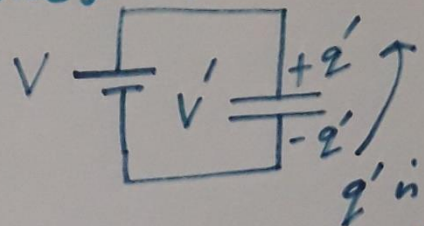

transferred

dW is needed for extra dq' transferred betⁿ the plates

$$V' = \frac{dW}{dq'}$$

$$dW = V' dq' = \frac{q'}{C} dq'$$

$$W = \int dW = \int_{q'=0}^{q'} \frac{q'}{C} dq' = \frac{1}{C} \int_0^q q' dq'$$

$$= \frac{1}{C} \left[\frac{q'^{1+1}}{1+1} \right]_0^q = \frac{1}{C} \left[\frac{q'^2}{2} \right]_0^q$$

$$= \frac{1}{2C} [q'^2]_0^q = \frac{1}{2C} (q^2 - 0^2)$$

$$W = \frac{1}{2C} q^2$$

$$U = W = \frac{1}{2C} q^2$$

[Work, W is stored as a potential energy, U]

$$U = \frac{q^2}{2C}$$

$$= \frac{(CV)^2}{2C}$$

$$= \frac{C^2 V^2}{2C}$$

$$= \frac{CV^2}{2}$$

$$U = \frac{1}{2} CV^2$$

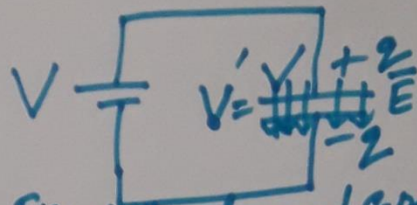


Fig fully charged capacitor
 $q = CV$

$$\therefore U = \frac{q^2}{2C} = \frac{1}{2} CV^2$$

Energy density u : Energy density is the potential energy per unit volume betⁿ the plates.

$$u = \frac{U}{V} = \frac{U}{Ad} = \left(\frac{1}{2} CV^2 \right) \frac{1}{Ad}$$

$$= \left(\frac{V^2}{2Ad} \right) C = \frac{V^2}{2Ad} \left(\frac{\epsilon_0 A}{d} \right)$$

$$= \frac{\epsilon_0 V^2}{2d^2} = \frac{1}{2} \epsilon_0 \left(\frac{V}{d} \right)^2$$

$$u = \frac{1}{2} \epsilon_0 E^2$$

$$[C = \frac{\epsilon_0 A}{d}]$$

$$[E = \frac{V}{d}]$$

Problem 29 (Book chapter 25):

What capacitance is required to store an energy of 10 kW.h at a potential difference of 1000 V?

Answer:

Given:

$$U = 10 \text{ kW}. h = 10000 \times 60 \times 60 \text{ Watt} - s$$

$$U = 36 \times 10^6 \frac{J}{s} s = 36 \times 10^6 \text{ J}$$

$$\text{Potential difference, } V = 1000 \text{ volt}$$

$$C = ?$$

$$[P = \frac{W}{t}]$$

$$\text{Unit: Watt} = \frac{J}{s}]$$

$$U = \frac{1}{2} CV^2$$

$$C = \frac{2U}{V^2} = \frac{2 \times 36 \times 10^6}{(1000)^2} = 72 \text{ F}$$

Problem 31 (Book chapter 25):

A $2.0 \mu\text{F}$ capacitor and a $4.0 \mu\text{F}$ capacitor are connected in parallel across a 300 V potential difference. Calculate the total energy stored in the capacitors.

Given

Answer:

$$C_1 = 2 \mu\text{F} \quad \text{and} \quad C_2 = 4 \mu\text{F}$$

C_1 and C_2 are in parallel

$$V = 300 \text{ volt}$$

$$C_{12} = C_1 + C_2 = 2 + 4 = 6 \mu\text{F} = 6 \times 10^{-6} \text{ F}$$

$U = ?$

We know

$$U = \frac{1}{2} C_{12} V^2 = \frac{6 \times 10^{-6} \times (300)^2}{2}$$

$$U = 0.27 \text{ J}$$

Problem 33 (Book chapter 25):

A charged isolated metal sphere of diameter 10 cm has a potential of 8000 V relative to $V = 0$ at infinity. Calculate the energy density in the electric field near the surface of the sphere.

Answer: next slide

Problem 33 (Book chapter 25):

Answer:

$$u = \frac{1}{2} \epsilon_0 \left(\frac{V}{R} \right)^2 = \frac{8.854 \times 10^{-12} \times (8000)^2}{2 \times (0.05)^2}$$

$$u = \frac{566.66 \times 10^{-6}}{5 \times 10^{-3}} = 113.33 \times 10^{-3} \frac{J}{m^3}$$

Sample problem 25.04 (page-730):

Answer:

We know

$$U = \frac{q^2}{2C}$$

For isolated sphere, $C = 4\pi\epsilon_0 R$

$$U = \frac{q^2}{2 \times 4\pi\epsilon_0 R} = \frac{9 \times 10^9 \times (1.25 \times 10^{-9})^2}{2 \times 0.0685}$$

$$U = 102.64 \times 10^{-9} J$$

$$u = \frac{1}{2} \epsilon_0 E^2 = \frac{8.854 \times 10^{-12}}{2} \left(\frac{q}{4\pi\epsilon_0 R^2} \right)^2 = \frac{8.854 \times 10^{-12}}{2} \left(\frac{9 \times 10^9 \times 1.25 \times 10^{-9}}{(0.0685)^2} \right)^2$$

$$u = \frac{1120.58 \times 10^{-12}}{4.403 \times 10^{-5}} = 25.450 \times 10^{-6} \frac{J}{m^3}$$

Given

For isolated sphere:

Diameter, $D = 10 \text{ cm}$

Radius, $R = 5 \text{ cm} = 0.05 \text{ m}$

$V = 8000 \text{ volt}$

$u = ?$

Given

For isolated sphere:

Radius, $R = 6.85 \text{ cm} = 0.0685 \text{ m}$

$q = 1.25 \text{ nC} = 1.25 \times 10^{-9} \text{ C}$

(a) $U = ?$

(b) $u = ?$

Thank You